

Finals Quiz 2 (total of 30 pts.)


Specify the type of logic gate of the following symbols: (2 pts. each)



1. OR GATE



2. AND GATE

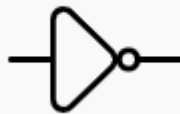

3. NOT GATE




4. NAND GATE



5. XOR GATE

Indicate the Boolean expression and output of the following logic diagrams. (10 points each)

1.

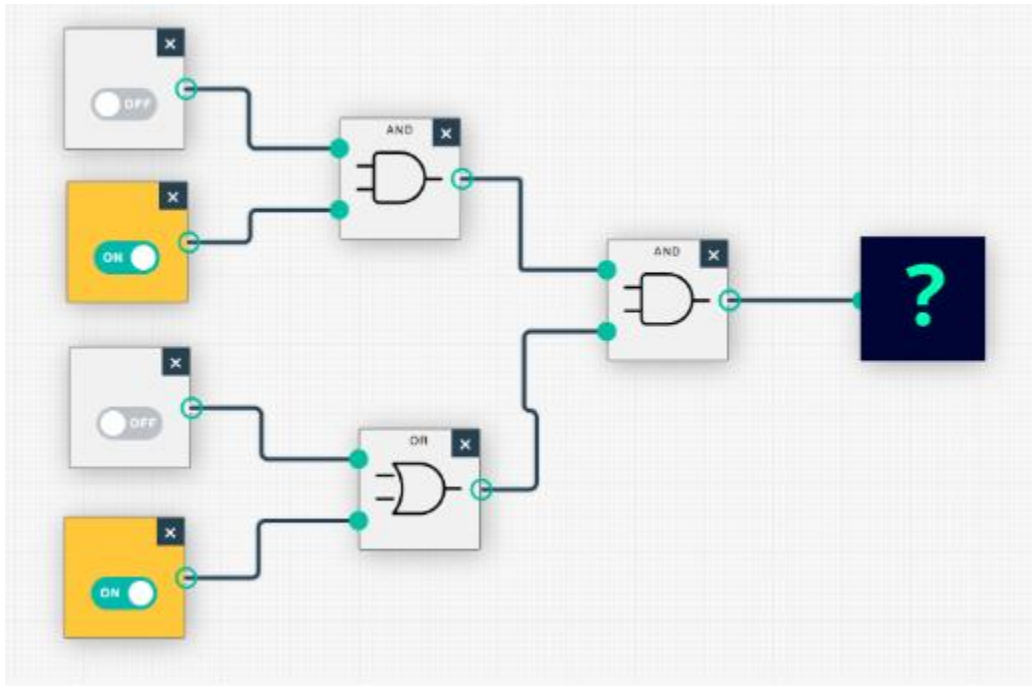


$$Q = (\sim A \cdot B) (\sim C + D)$$

$$Q = (0 \cdot 1) (0 + 1)$$

$$Q = (0)(1)$$

$$Q = 0$$


2.

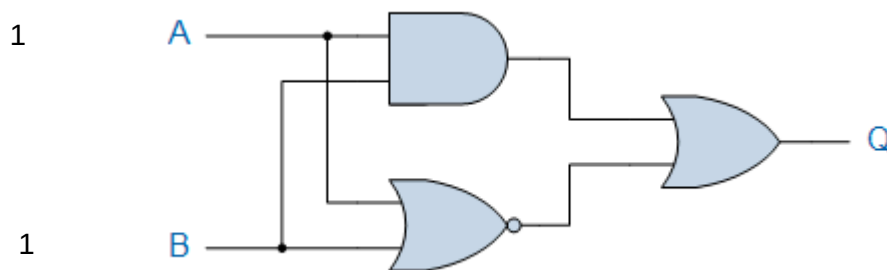

$$Q = (A \cdot B) + (\sim(A+B))$$

$$Q = (1) + (0)$$

$$Q = 1$$

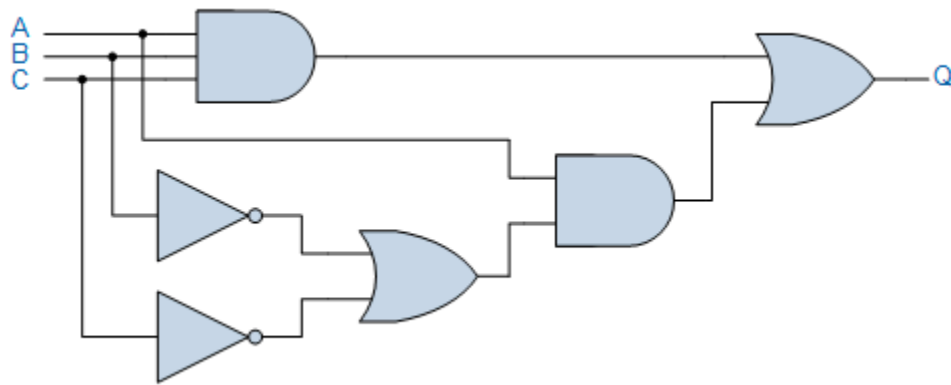

1.

GIVEN EQUATION: $Q = (A.B.C) + (A . (\bar{B} + \bar{C}))$

Q = wala pa binibigay si mam na value sa abc kaya piniem ko muna